

Lab5 流水线 CPU 设计

李远航

PB20000137


1. 实验目标

- 理解流水线 CPU 的结构和工作原理
- 掌握流水线 CPU 的设计和调试方法，特别是流水线中数据相关和控制相关的处理
- 熟练掌握数据通路和控制器的设计和描述方法


2. 实验环境

- PC 一台
- Vivado 2020.2
- fpgaol.ustc.edu.cn

3. 逻辑结构

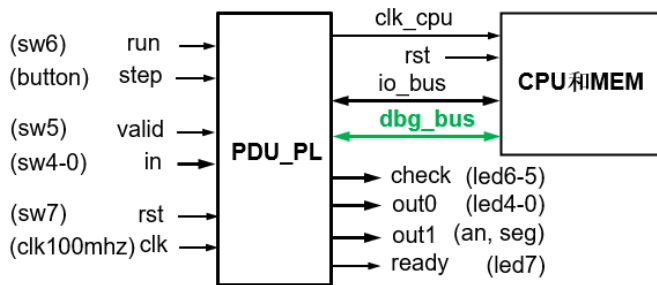

4. 数据通路

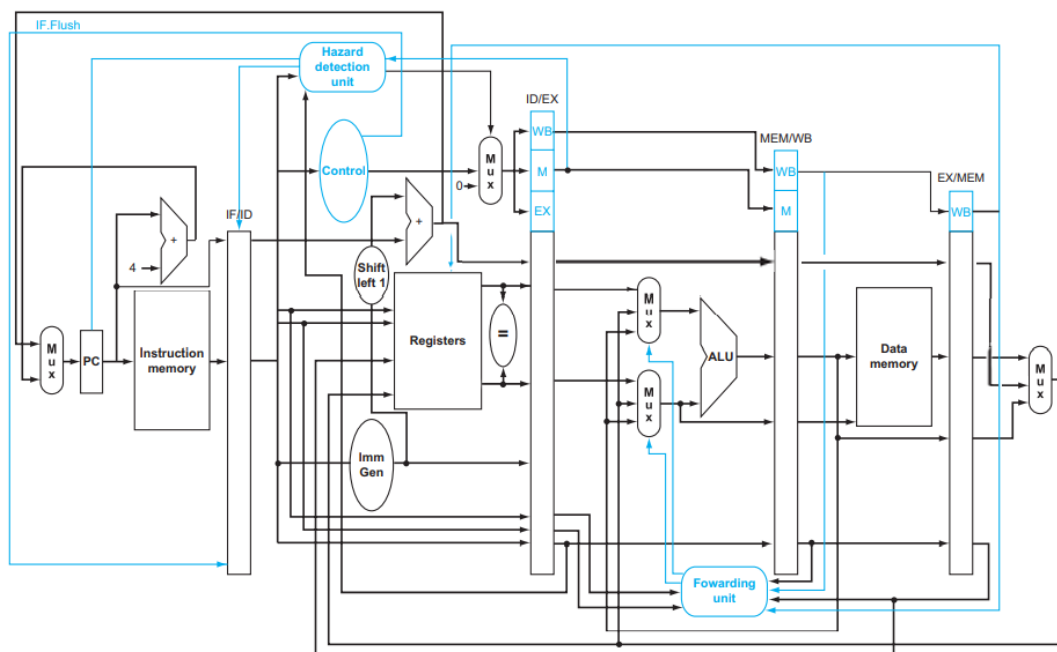

在课本数据的路基基础上，传递 pc+4 给寄存器写回选择器

5. 具体实现

a) 无冒险流水线 cpu

在单周期流水线的基础下，加入流水线段寄存器(处理冒险会对段寄存器进行一定的修改，具体见最后源码)

b) 数据冒险

1. ForWarding

```
module Forwarding(  
    input [31:0] ins_EX,  
    input [31:0] ins_MEM,  
    input [31:0] ins_WB,  
    input RegWrite_MEM, RegWrite_WB,  
    output reg [1:0] alu_rs1_mux_signal,  
    output reg [1:0] alu_rs2_mux_signal  
);  
    always@(*) begin  
        if(RegWrite_MEM && ins_MEM[11:7]==ins_EX[19:15])  
            alu_rs1_mux_signal = 2'b01;  
        else if(RegWrite_WB && ins_WB[11:7]==ins_EX[19:15])  
            alu_rs1_mux_signal = 2'b10;  
        else  
            alu_rs1_mux_signal = 2'b00;  
  
        if(RegWrite_MEM && ins_MEM[11:7]==ins_EX[24:20])  
            alu_rs2_mux_signal = 2'b01;  
        else if(RegWrite_WB && ins_WB[11:7]==ins_EX[24:20])  
            alu_rs2_mux_signal = 2'b10;  
        else  
            alu_rs2_mux_signal = 2'b00;  
    end  
endmodule
```

在 alu 的操作数前加入选择器，根据是否发生前递来选择 alu 的操作数，控制信号如上所示

2. stall

```
module stall(  
    input MemRead_EX, Branch_ID, RegWrite_EX, RegWrite_MEM, RegWrite_WB,  
    input [31:0] ins_EX,  
    input [31:0] ins_ID,  
    input [31:0] ins_MEM,  
    input [31:0] ins_WB,  
    output reg pc_write, IF_ID_write, control_mux, jump  
);  
    always@(*) begin  
        if(MemRead_EX &&  
(ins_EX[11:7]==ins_ID[19:15] || ins_EX[11:7]==ins_ID[24:20])) begin
```

```

        pc_write = 0;
        IF_ID_write = 0;
        control_mux = 1;
        jump = 0;
    end
    else begin
        pc_write = 1;
        IF_ID_write = 1;
        control_mux = 0;
        jump = 0;
    end
end
endmodule

```

判断是否需要 stall，如果需要 stall，则 IF_ID 寄存器下一个时钟周期内不向后传递数据，ID_EX 寄存器向后传递的数据为 0

3. 控制冒险

```


//判断阻塞
else if(Branch_ID && RegWrite_EX &&
(ins_EX[11:7]==ins_ID[19:15]||ins_EX[11:7]==ins_ID[24:20])) begin
    pc_write = 0;
    IF_ID_write = 0;
    control_mux = 1;
    jump = 0;
end
else if(Branch_ID && RegWrite_MEM &&
(ins_MEM[11:7]==ins_ID[19:15]||ins_MEM[11:7]==ins_ID[24:20])) begin
    pc_write = 0;
    IF_ID_write = 0;
    control_mux = 1;
    jump = 0;
end
//判断是否需要跳转，同时将jump信号传递给IF_ID段寄存器
assign jump = (jump_branch && Read_data_1_ID==Read_data_2_ID)||jal_ID;
mux2to1 pc_mux(
    .a(pc_4_IF),
    .b(pc_offset_ID),
    .sel(jump),
    .out(next_pc)
);

```


分支指令需要取的寄存器即将被写入，则直接 stall 到该寄存器可以取用的 WB 阶段，然后直接在 ID 阶段判断跳转，如果需要跳转，则将此时写入 IF 的指令 flush 掉

6. 运行截图

1. harzards_test.s

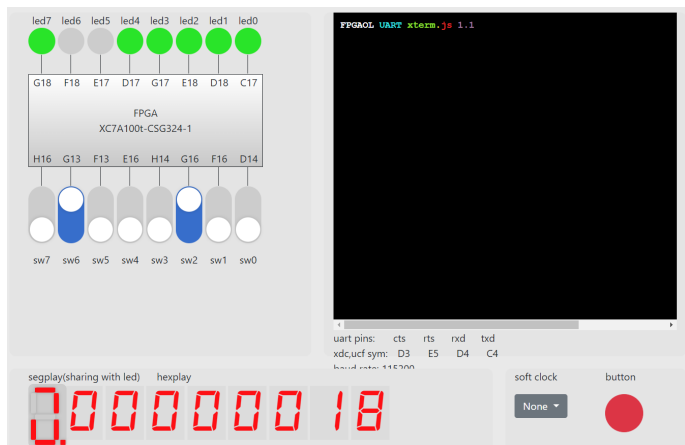

2. fib_test.s

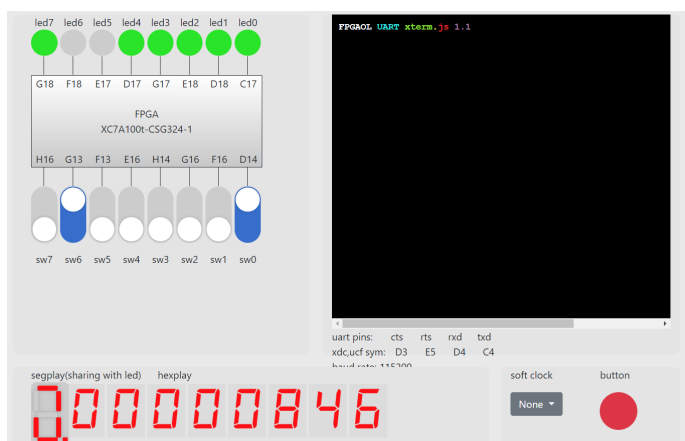

7. 实验收获

- 理解了流水线 CPU 的结构和工作原理
- 掌握了流水线 CPU 的设计和调试方法
- 掌握了数据通路和控制器的设计和描述方法
- 对流水线的冒险处理有的更深的认识

8. 源码

```
module top(
    input run, step, valid, rst, clk,
    input [4:0] in,
    output [1:0] check,
    output [4:0] out0,

    // output [31:0] pcin, pc, pcd, pce,
    // output [31:0] ir, imm, mdr,
    // output [31:0] a, b, y, bm, yw,
    // output [4:0] rd, rdm, rdw,
    // output [31:0] ctrl, ctrlm, ctrlw,

    output ready,
    output [2:0] an,
```

```

output [3:0] seg
);

wire clk_cpu;

//IO_BUS
wire [7:0] io_addr;
wire [31:0] io_dout;
wire io_we;
wire [31:0] io_din;

//Debug_BUS
wire [7:0] m_rf_addr;
wire [31:0] rf_data;
wire [31:0] m_data;

wire [31:0] pcin, pc, pcd, pce;
wire [31:0] ir, imm, mdr;
wire [31:0] a, b, y, bm, yw;
wire [4:0] rd, rdm, rdw;
wire [31:0] ctrl, ctrlm, ctrlw;

pdu pdu(
    .clk(clk),
    .rst(rst),
    .run(run),
    .step(step),
    .clk_cpu(clk_cpu),
    .valid(valid),
    .in(in),
    .check(check),
    .out0(out0),
    .an(an),
    .seg(seg),
    .ready(ready),
    .io_addr(io_addr),
    .io_dout(io_dout),
    .io_we(io_we),
    .io_din(io_din),
    .m_rf_addr(m_rf_addr),
    .rf_data(rf_data),
    .m_data(m_data),
    .pcin(pcin),
    .pc(pc),
    .pcd(pcd),
    .pce(pce),
    .ir(ir),
    .imm(imm),
    .mdr(mdr),
    .a(a),
    .b(b),
    .y(y),
    .bm(bm),
    .yw(yw),

```

```

        .rd(rd),
        .rdm(rdm),
        .rdw(rdw),
        .ctrl(ctrl),
        .ctrlm(ctrlm),
        .ctrlw(ctrlw)
    );

```

```

cpu_pipeline cpu_pipeline(
    .clk(clk_cpu),
    .rst(rst),
    .io_addr(io_addr),
    .io_dout(io_dout),
    .io_we(io_we),
    .io_din(io_din),
    .m_rf_addr(m_rf_addr),
    .rf_data(rf_data),
    .m_data(m_data),
    .pcin(pcin),
    .pc(pc),
    .pcd(pcd),
    .pce(pce),
    .ir(ir),
    .imm(imm),
    .mdr(mdr),
    .a(a),
    .b(b),
    .y(y),
    .bm(bm),
    .yw(yw),
    .rd(rd),
    .rdm(rdm),
    .rdw(rdw),
    .ctrl(ctrl),
    .ctrlm(ctrlm),
    .ctrlw(ctrlw)
);

```

endmodule

```

module cpu_pipeline(
    input clk,rst,
    output [7:0] io_addr,
    output [31:0] io_dout,
    output io_we,
    input [31:0] io_din,

    input [7:0] m_rf_addr,
    output [31:0] rf_data,
    output [31:0] m_data,

    output [31:0] pcin, pc, pcd, pce,
    output [31:0] ir, imm, mdr,
    output [31:0] a, b, y, bm, yw,
    output [4:0] rd, rdm, rdw,

```

```

    output [31:0] ctrl, ctrlm, ctrlw
);
    wire [31:0] pc_IF, pc_ID, pc_EX, pc_MEM, pc_WB;
    wire [31:0] pc_4_IF, pc_4_ID, pc_4_EX, pc_4_MEM, pc_4_WB;
    wire [31:0] pc_offset_IF, pc_offset_ID, pc_offset_EX, pc_offset_MEM,
pc_offset_WB;
    wire [31:0] ins_IF, ins_ID, ins_EX, ins_MEM, ins_WB;
    wire [31:0] alu_result_IF, alu_result_ID, alu_result_EX, alu_result_MEM,
alu_result_WB;
    wire alu_zero_IF, alu_zero_ID, alu_zero_EX, alu_zero_MEM, alu_zero_WB;
    wire [31:0] Read_data_1_IF, Read_data_1_ID, Read_data_1_EX, Read_data_1_MEM,
Read_data_1_WB;
    wire [31:0] Read_data_2_IF, Read_data_2_ID, Read_data_2_EX, Read_data_2_MEM,
Read_data_2_WB;
    wire [31:0] memory_read_data, memory_read_data_IF, memory_read_data_ID,
memory_read_data_EX, memory_read_data_MEM, memory_read_data_WB;
    wire [31:0] Write_data_IF, Write_data_ID, Write_data_EX, Write_data_MEM,
Write_data_WB;
    wire [31:0] immediate_num_IF, immediate_num_ID, immediate_num_EX,
immediate_num_MEM, immediate_num_WB;
    wire [31:0] alu_op1, alu_op2;
    wire [2:0] alu_control;
    wire [31:0] next_pc;

    wire Branch_ID, MemRead_ID, MemWrite_ID, RegWrite_ID, ALUsrc_ID, jal_ID;
    wire [1:0] ALUop_ID, MemtoReg_ID;
    wire Branch_EX, MemRead_EX, MemWrite_EX, RegWrite_EX, ALUsrc_EX, jal_EX;
    wire [1:0] ALUop_EX, MemtoReg_EX;
    wire Branch_MEM, MemRead_MEM, MemWrite_MEM, RegWrite_MEM, ALUsrc_MEM, jal_MEM;
    wire [1:0] ALUop_MEM, MemtoReg_MEM;
    wire Branch_WB, MemRead_WB, MemWrite_WB, RegWrite_WB, ALUsrc_WB, jal_WB;
    wire [1:0] ALUop_WB, MemtoReg_WB;
    wire [1:0] alu_rs1_mux_signal, alu_rs2_mux_signal;
    wire [31:0] alu_rs1_fw, alu_rs2_fw;

    wire pc_write, IF_ID_write, control_mux;
    wire jump_branch, jump;

    assign pc = pc_IF;
    assign pcd = pc_ID;
    assign ir = ins_ID;
    assign pcin = next_pc;
    assign pce = pc_EX;
    assign a = alu_rs1_fw;
    assign b = alu_rs2_fw;
    assign imm = immediate_num_EX;
    assign rd = ins_EX[11:7];
    assign ctrl =
{~IF_ID_write,~control_mux,jump,3'b0,alu_rs1_mux_signal,2'b0,alu_rs2_mux_signal,1'
b0,RegWrite_ID,MemtoReg_ID,2'b0,MemRead_ID,MemWrite_ID,2'b0,jal_ID,Branch_ID,2'b0,
alu_rs1_mux_signal,alu_rs2_mux_signal,ALUop_ID};
    assign y = alu_result_MEM;
    assign bm = Read_data_2_MEM;
    assign rdm = ins_MEM[11:7];

```

```

    assign ctrlm =
    {~IF_ID_write,~control_mux,jump,3'b0,alu_rs1_mux_signal,2'b0,alu_rs2_mux_signal,1'
b0,RegWrite_MEM,MemtoReg_MEM,2'b0,MemRead_MEM,MemWrite_MEM,2'b0,jal_MEM,Branch_MEM
,2'b0,alu_rs1_mux_signal,alu_rs2_mux_signal,ALUop_MEM};
    assign yw = alu_result_WB;
    assign mdr = memory_read_data_WB;
    assign rdw = ins_WB[11:7];
    assign ctrlw =
    {~IF_ID_write,~control_mux,jump,3'b0,alu_rs1_mux_signal,2'b0,alu_rs2_mux_signal,1'
b0,RegWrite_WB,MemtoReg_WB,2'b0,MemRead_WB,MemWrite_WB,2'b0,jal_WB,Branch_WB,2'b0,
alu_rs1_mux_signal,alu_rs2_mux_signal,ALUop_WB};

    // assign temp1 = alu_rs1_mux_signal;
    // assign temp2 = alu_rs2_mux_signal;
    // assign temp0 = {27'b0,ins_EX[11:7]};
    // assign temp = {27'b0,ins_ID[19:15]};
    // assign temp1 = IF_ID_write;
    // assign temp2 = pc_write;
    // assign temp3 = control_mux;

    pc pc_reg(
        .in(next_pc),
        .rst(rst),
        .clk(clk),
        .en(pc_write),
        .out(pc_IF)
    );

    add pc_add(
        .a(pc_IF),
        .b(32'd4),
        .out(pc_4_IF)
    );

    dist_mem_gen_3 Instruction_memory (
        .clk(clk),
        .we(1'b0),
        .d(0),
        .a(pc_IF[9:2]),
        .spo(ins_IF)
    );

    dist_mem_gen_1 Data_memory (
        .a(alu_result_MEM[9:2]),
        .d(Read_data_2_MEM),
        .dpra(m_rf_addr),
        .clk(clk),
        .we(MemWrite&&(~alu_result_MEM[10])),
        .spo(memory_read_data),
        .dpo(m_data)
    );

```



```

register reg_file(
    .clk(clk),
    .rst(rst),
    .w_en(RegWrite_WB||jal_WB),
    .addr1(ins_ID[19:15]),
    .addr2(ins_ID[24:20]),
    .addr3(ins_WB[11:7]),
    .w_data3(Write_data_WB),
    .rd_data1(Read_data_1_ID),
    .rd_data2(Read_data_2_ID),
    .debug_addr(m_rf_addr),
    .debug_data(rf_data)
);

Immgen Immgen(
    .instruction(ins_ID),
    .immediate(immediate_num_ID)
);

control control(
    .ins(ins_ID[6:0]),
    .Branch(Branch_ID),
    .MemRead(MemRead_ID),
    .MemtoReg(MemtoReg_ID),
    .MemWrite(MemWrite_ID),
    .ALUsrc(ALUsrc_ID),
    .RegWrite(RegWrite_ID),
    .ALUop(ALUop_ID),
    .jal(jal_ID)
);

IF_ID IF_ID(
    .clk(clk),
    .rst(rst),
    .en(IF_ID_write),
    .jump(jump),
    .ins(ins_IF),
    .pc(pc_IF),
    .pc_4(pc_4_IF),
    .ins_o(ins_ID),
    .pc_o(pc_ID),
    .pc_4_o(pc_4_ID)
);

ID_EX ID_EX(
    .clk(clk),
    .rst(rst),
    .en(control_mux),
    .ins(ins_ID),
    .immediate(immediate_num_ID),
    .pc(pc_ID),
    .pc_4(pc_4_ID),
    .rd1(Read_data_1_ID),
    .rd2(Read_data_2_ID),

```

```

        .ins_o(ins_EX),
        .immediate_o(immediate_num_EX),
        .pc_o(pc_EX),
        .pc_4_o(pc_4_EX),
        .rd1_o(Read_data_1_EX),
        .rd2_o(Read_data_2_EX),
        .Branch(Branch_ID),
        .MemRead(MemRead_ID),
        .MemtoReg(MemtoReg_ID),
        .MemWrite(MemWrite_ID),
        .ALUsrc(ALUsrc_ID),
        .RegWrite(RegWrite_ID),
        .ALUop(ALUop_ID),
        .jal(jal_ID),
        .Branch_o(Branch_EX),
        .MemRead_o(MemRead_EX),
        .MemtoReg_o(MemtoReg_EX),
        .MemWrite_o(MemWrite_EX),
        .ALUsrc_o(ALUsrc_EX),
        .RegWrite_o(RegWrite_EX),
        .ALUop_o(ALUop_EX),
        .jal_o(jal_EX)
    );

```

```

EX_MEM EX_MEM(
    .clk(clk),
    .rst(rst),
    .pc_4(pc_4_EX),
    .pc_offset(pc_offset_EX),
    .alu_result(alu_result_EX),
    .alu_zero(alu_zero_EX),
    .rd2(alu_rs2_fw),
    .ins(ins_EX),
    .pc_4_o(pc_4_MEM),
    .pc_offset_o(pc_offset_MEM),
    .alu_result_o(alu_result_MEM),
    .alu_zero_o(alu_zero_MEM),
    .rd2_o(Read_data_2_MEM),
    .ins_o(ins_MEM),
    .Branch(Branch_EX),
    .MemRead(MemRead_EX),
    .MemtoReg(MemtoReg_EX),
    .MemWrite(MemWrite_EX),
    .RegWrite(RegWrite_EX),
    .jal(jal_EX),
    .Branch_o(Branch_MEM),
    .MemRead_o(MemRead_MEM),
    .MemtoReg_o(MemtoReg_MEM),
    .MemWrite_o(MemWrite_MEM),
    .RegWrite_o(RegWrite_MEM),
    .jal_o(jal_MEM)
);

```

```

MEM_WB MEM_WB(

```

```

        .clk(clk),
        .rst(rst),
        .alu_result(alu_result_MEM),
        .ins(ins_MEM),
        .MemReadData(memory_read_data_MEM),
        .pc_4(pc_4_MEM),
        .alu_result_o(alu_result_WB),
        .ins_o(ins_WB),
        .MemReadData_o(memory_read_data_WB),
        .pc_4_o(pc_4_WB),
        .MemtoReg(MemtoReg_MEM),
        .RegWrite(RegWrite_MEM),
        .MemtoReg_o(MemtoReg_WB),
        .RegWrite_o(RegWrite_WB)
    );

    assign alu_op1 = alu_rs1_fw;
    mux3to1 alu_rs1_mux(
        .a(Read_data_1_EX),
        .b(alu_result_MEM),
        .c(Write_data_WB),
        .sel(alu_rs1_mux_signal),
        .out(alu_rs1_fw)
    );

    mux3to1 alu_rs2_mux(
        .a(Read_data_2_EX),
        .b(alu_result_MEM),
        .c(Write_data_WB),
        .sel(alu_rs2_mux_signal),
        .out(alu_rs2_fw)
    );

    Forwarding Forwarding(
        .ins_EX(ins_EX),
        .ins_MEM(ins_MEM),
        .ins_WB(ins_WB),
        .RegWrite_MEM(RegWrite_MEM),
        .RegWrite_WB(RegWrite_WB),
        .alu_rs1_mux_signal(alu_rs1_mux_signal),
        .alu_rs2_mux_signal(alu_rs2_mux_signal)
    );

    stall stall(
        .MemRead_EX(MemRead_EX),
        .Branch_ID(Branch_ID),
        .RegWrite_EX(RegWrite_EX),
        .RegWrite_MEM(RegWrite_MEM),
        .RegWrite_WB(RegWrite_WB),
        .ins_EX(ins_EX),
        .ins_ID(ins_ID),
        .ins_MEM(ins_MEM),
        .ins_WB(ins_WB),
        .pc_write(pc_write),

```

```

        .IF_ID_write(IF_ID_write),
        .control_mux(control_mux),
        .jump(jump_branch)
    );

mux2to1 alu_mux(
    .a(alu_rs2_fw),
    .b(immediate_num_EX),
    .sel(ALUsrc_EX),
    .out(alu_op2)
);

alucontrol alucontrol(
    .ALUOp(ALUop_EX),
    .ALUout(alu_control),
    .funct7(ins_EX[31:25])
);

alu alu(
    .a(alu_op1),
    .b(alu_op2),
    .f(alu_control),
    .z_r(alu_zero_EX),
    .y_r(alu_result_EX)
);

mux2to1 sw_lw_mux(
    .a(memory_read_data),
    .b(io_din[31:0]),
    .sel(alu_result_MEM[10]),
    .out(memory_read_data_MEM)
);

mux3to1 reg_mux(
    .a(alu_result_WB),
    .b(memory_read_data_WB),
    .c(pc_4_WB),
    .sel(MemtoReg_WB),
    .out(Write_data_WB)
);

wire [31:0] shiftright_already;
shiftright shiftright(
    .in(immediate_num_ID),
    .out(shiftright_already)
);

add pc_add_offset(
    .a(pc_ID),
    .b(shiftright_already),
    .out(pc_offset_ID)
);

// assign jump = (Branch_ID&&Read_data_1_ID==Read_data_2_ID)||jal_ID;

```

```

// assign IF_ID_write_jump = (jump == 1) ? 0 : 1;
// assign temp = jump;
// assign jump_r = jump;
assign jump = (jump_branch && Read_data_1_ID==Read_data_2_ID)||jal_ID;
// assign jump_r = jump;
mux2to1 pc_mux(
    .a(pc_4_IF),
    .b(pc_offset_ID),
    .sel(jump),
    .out(next_pc)
);

assign io_addr = alu_result_MEM[7:0];
assign io_dout = Read_data_2_MEM;
assign io_we = MemWrite_MEM&&(alu_result_MEM[10]);
endmodule

module pdu(
    input clk,
    input rst,

    //选择CPU工作方式;
    input run,
    input step,
    output clk_cpu,

    //输入switch的端口
    input valid,
    input [4:0] in,

    //输出led和seg的端口
    output [1:0] check, //led6-5:查看类型
    output [4:0] out0, //led4-0
    output [2:0] an, //8个数码管
    output [3:0] seg,
    output ready, //led7

    //IO_BUS
    input [7:0] io_addr,
    input [31:0] io_dout,
    input io_we,
    output [31:0] io_din,

    //Debug_BUS
    output reg[7:0] m_rf_addr,
    input [31:0] rf_data,
    input [31:0] m_data,

    //增加流水线寄存器调试接口
    input [31:0] pcin, pc, pcd, pce,
    input [31:0] ir, imm, mdr,
    input [31:0] a, b, y, bm, yw,
    input [4:0] rd, rdm, rdw,
    input [31:0] ctrl, ctrlm, ctrlw
);

```

```

reg [4:0] in_r, in_2r;    //同步外部输入用，为信号in增加一级寄存器
reg run_r, step_r, step_2r, valid_r, valid_2r;
wire step_p, valid_pn;    //取边沿信号
wire pre_pn,next_pn;      //增加取边沿信号

reg clk_cpu_r;           //寄存器输出CPU时钟
reg [4:0] out0_r;         //输出外设端口
reg [31:0] out1_r;
reg ready_r;
reg [19:0] cnt;           //刷新计数器，刷新频率约为95Hz
reg [1:0] check_r;       //查看信息类型，00-运行结果，01-寄存器堆，10-存储器，11-plr

reg [7:0] io_din_a; //_a表示为满足组合always描述要求定义的，下同
reg [4:0] out0_a;
reg [31:0] out1_a;
reg [3:0] seg_a;

//增加pre,next取边沿计数器
reg [4:0] cnt_m_rf;       //寄存器堆和存储器地址计数器
reg [1:0] cnt_ah_plr;     //流水线寄存器高两位地址计数器
reg [2:0] cnt_al_plr;     //流水线寄存器低三位地址计数器

//增加流水线寄存器地址和数据选择输入
wire [4:0] addr_plr ;
reg [31:0] plr_data;

assign clk_cpu = clk_cpu_r;
assign io_din = io_din_a;
assign check = check_r;
assign out0 = out0_a;
assign ready = ready_r;
assign seg = seg_a;
assign an = cnt[19:17];
assign step_p = step_r & ~step_2r;    //取上升沿
assign valid_pn = valid_r ^ valid_2r; //取上升沿或下降沿
assign pre_pn = in_r[1] ^ in_2r[1];    //增加pre取上升或下降沿信号
assign next_pn = in_r[0] ^ in_2r[0];   //增加next取上升或下降沿信号

//同步输入信号
always @(posedge clk) begin
    run_r <= run;
    step_r <= step;
    step_2r <= step_r;
    valid_r <= valid;
    valid_2r <= valid_r;
    in_r <= in;
    in_2r <= in_r;    //为信号in增加一级寄存器
end

//CPU工作方式
always @(posedge clk, posedge rst) begin
    if(rst)
        clk_cpu_r <= 0;

```

```

    else if (run_r)
        clk_cpu_r <= ~clk_cpu_r;
    else
        clk_cpu_r <= step_p;
end

//读外设端口
always @* begin
    case (io_addr)
        8'h0c: io_din_a = {{27{1'b0}}, in_r};
        8'h10: io_din_a = {{31{1'b0}}, valid_r};
        default: io_din_a = 32'h0000_0000;
    endcase
end

//写外设端口
always @(posedge clk, posedge rst) begin
    if (rst) begin
        out0_r <= 5'h1f;
        out1_r <= 32'h1234_5678;
        ready_r <= 1'b1;
    end
    else if (io_we)
        case (io_addr)
            8'h00: out0_r <= io_dout[4:0];
            8'h04: ready_r <= io_dout[0];
            8'h08: out1_r <= io_dout;
            default: ;
        endcase
    end

//增加寄存器堆和存储器地址计数：依靠pre,next边沿计数使能
always @(posedge clk, posedge rst) begin
    if (rst) cnt_m_rf <= 5'b0_0000;
    else if (step_p)
        cnt_m_rf <= 5'b0_0000;
    else if (next_pn)
        cnt_m_rf <= cnt_m_rf + 5'b0_0001;
    else if (pre_pn)
        cnt_m_rf <= cnt_m_rf - 5'b0_0001;
end

//增加流水寄存器地址计数，流水线寄存器高两位地址依靠pre边沿计数，低三位地址依靠next边沿计数
always @(posedge clk, posedge rst) begin
    if (rst) cnt_ah_plr <= 2'b00;
    else if (step_p)
        cnt_ah_plr <= 2'b00;
    else if (pre_pn)
        cnt_ah_plr <= cnt_ah_plr + 2'b01;
end

always @(posedge clk, posedge rst) begin
    if (rst) cnt_al_plr <= 3'b000;

```

```

else if (step_p)
    cnt_al_plr <= 3'b000;
else if (next_pn)
    if (cnt_ah_plr==2'b01)
        if (cnt_al_plr == 3'b101)
            cnt_al_plr <= 3'b000;
        else cnt_al_plr <= cnt_al_plr + 3'b001;
    else begin
        cnt_al_plr [2] <= 1'b0;
        cnt_al_plr [1:0] <= cnt_al_plr[1:0] + 2'b01;
    end
end

assign  addr_plr = {cnt_ah_plr,cnt_al_plr}; //增加流水线寄存器地址

//寄存器堆和存储器地址输出选择
//下面的always块也可以用assign m_rf_addr = {in_r[4:2],cnt_m_rf};代替因为寄存器堆只需要低5位就可以了，不关心高3位
always @(*) begin
    case (check_r[1])
        1'b0:
            m_rf_addr = {3'b000,cnt_m_rf};
        1'b1:
            m_rf_addr = {in_r[4:2],cnt_m_rf};
    endcase
end

//流水线寄存器数据选择输入
always @(*)begin
    case (cnt_ah_plr)
        //PC/IF/ID
        2'b00:
            case (cnt_al_plr[1:0])
                2'b00: plr_data = pc;
                2'b01: plr_data = pcd;
                2'b10: plr_data = ir;
                2'b11: plr_data = pcin;
            endcase
        //ID/EX
        2'b01:
            begin
                case (cnt_al_plr)
                    3'b000: plr_data = pce;
                    3'b001: plr_data = a;
                    3'b010: plr_data = b;
                    3'b011: plr_data = imm;
                    3'b100: plr_data = {{27{1'b0}},rd};
                    3'b101: plr_data = ctrl;
                    default: plr_data = pce;
                endcase
            end
        //EX/MEM
        2'b10:
            case (cnt_al_plr[1:0])

```



```

    2'b00: plr_data = y;
    2'b01: plr_data = bm;
    2'b10: plr_data = {{27{1'b0}},rdm};
    2'b11: plr_data = ctrlm;
endcase
//MEM/WB
2'b11:
    case (cnt_al_plr[1:0])
    2'b00: plr_data = yw;
    2'b01: plr_data = mdr;
    2'b10: plr_data = {{27{1'b0}},rdw};
    2'b11: plr_data = ctrlw;
    endcase
endcase
end

//LED和数码管查看类型
always @(posedge clk, posedge rst) begin
if(rst)
    check_r <= 2'b00;
else if(run_r)
    check_r <= 2'b00;
else if (step_p)
    check_r <= 2'b00;
else if (valid_pn)
    check_r <= check - 2'b01;
end

//LED和数码管显示内容
always @(*)begin
    case (check_r)
    2'b00: begin
        out0_a = out0_r;
        out1_a = out1_r;
    end
    2'b01: begin
        out0_a = cnt_m_rf;
        out1_a = rf_data;
    end
    2'b10: begin
        out0_a = cnt_m_rf;
        out1_a = m_data;
    end
    2'b11: begin
        out0_a = addr_plr;
        out1_a = plr_data;    //更改为流水线寄存器地址和数据显示
    end
    endcase
end

//扫描数码管
always @(posedge clk, posedge rst) begin
    if (rst) cnt <= 20'h0_0000;
    else cnt <= cnt + 20'h0_0001;
end

```

```
end
```

```
always @* begin
    case (an)
        3'd0: seg_a = out1_a[3:0];
        3'd1: seg_a = out1_a[7:4];
        3'd2: seg_a = out1_a[11:8];
        3'd3: seg_a = out1_a[15:12];
        3'd4: seg_a = out1_a[19:16];
        3'd5: seg_a = out1_a[23:20];
        3'd6: seg_a = out1_a[27:24];
        3'd7: seg_a = out1_a[31:28];
        default: ;
    endcase
end
endmodule
```

```
module add(
    input [31:0] a, b,
    output reg[31:0] out
);
    always@(*)
        out = a + b;
endmodule
```

```
module alu(
    input [31:0] a, b,
    input [2:0] f,
    output reg z_r,
    output reg [31:0] y_r
);
    always@(*)begin
        case(f)
            3'b000: y_r = a + b;
            3'b001: y_r = a - b;
            3'b010: y_r = a & b;
            3'b011: y_r = a | b;
            3'b100: y_r = a ^ b;
            default: y_r = 0;
        endcase
        if (y_r == 0)
            z_r = 1;
        else
            z_r = 0;
        end
    end
endmodule
```

```
endmodule
```

```
module alucontrol (
    input [1:0] ALUOp,
    input [6:0] funct7,
    output reg [2:0] ALUout
);
    always@(*) begin
```

```

        case(ALUOp)
            2'b00: ALUout=3'b000;
            2'b01: ALUout=3'b001;
            2'b10: begin
                if(func7 == 7'b0000000)
                    ALUout = 3'b000;
                else if(func7 == 7'b0100000)
                    ALUout = 3'b001;
                else
                    ALUout = 3'b000;
            end
            default: ALUout = 3'b000;
        endcase
    end
endmodule

module control(
    input [6:0] ins,
    output reg Branch, MemRead, MemWrite, RegWrite, ALUsrc, jal,
    output reg [1:0] ALUOp, MemtoReg
);
    always @(*) begin
        case(ins)
            7'b0110011: begin //add
                Branch = 0;
                MemRead = 0;
                MemWrite = 0;
                RegWrite = 1;
                ALUsrc = 0;
                ALUOp = 2'b10;
                jal = 0;
                MemtoReg = 2'b0;
            end
            7'b0010011: begin //addi
                Branch = 0;
                MemRead = 0;
                MemWrite = 0;
                RegWrite = 1;
                ALUsrc = 1;
                ALUOp = 2'b10;
                jal = 0;
                MemtoReg = 2'b0;
            end
            7'b0000011: begin //lw
                Branch = 0;
                MemRead = 1;
                MemWrite = 0;
                RegWrite = 1;
                ALUsrc = 1;
                ALUOp = 2'b00;
                jal = 0;
                MemtoReg = 2'b01;
            end
            7'b0100011: begin //sw

```

```

        Branch = 0;
        MemRead = 0;
        MemWrite = 1;
        RegWrite = 0;
        ALUSrc = 1;
        ALUOp = 2'b00;
        jal = 0;
        MemtoReg = 2'b0;
    end
    7'b1100011: begin //beq
        Branch = 1;
        MemRead = 0;
        MemWrite = 0;
        RegWrite = 0;
        ALUSrc = 0;
        ALUOp = 2'b01;
        jal = 0;
        MemtoReg = 2'b0;
    end
    7'b1101111: begin //jal
        Branch = 0;
        MemRead = 0;
        MemWrite = 0;
        RegWrite = 1;
        ALUSrc = 0;
        ALUOp = 2'b00;
        jal = 1;
        MemtoReg = 2'b10;
    end
    default: begin
        Branch = 0;
        MemRead = 0;
        MemWrite = 0;
        RegWrite = 0;
        ALUSrc = 0;
        ALUOp = 2'b00;
        jal = 0;
        MemtoReg = 2'b0;
    end
endcase
end
endmodule

```

```

module EX_MEM(
    input clk,rst,
    input [31:0] pc_4,
    input [31:0] pc_offset,
    input [31:0] alu_result,
    input alu_zero,
    input [31:0] rd2,
    input [31:0] ins,
    output reg [31:0] pc_4_o,
    output reg [31:0] pc_offset_o,
    output reg [31:0] alu_result_o,

```

```

output reg alu_zero_o,
output reg [31:0] rd2_o,
output reg [31:0] ins_o,

input Branch, MemRead, MemWrite, RegWrite, jal,
input [1:0] MemtoReg,
output reg Branch_o, MemRead_o, MemWrite_o, RegWrite_o, jal_o,
output reg [1:0] MemtoReg_o
);

reg [31:0] pc_4_t, pc_offset_t, alu_result_t, rd2_t, ins_t;
reg alu_zero_t;
reg Branch_t, MemRead_t, MemWrite_t, RegWrite_t, jal_t;
reg [1:0] MemtoReg_t;

always@(posedge clk or posedge rst) begin
    if(rst) begin
        // pc_4_t <= 32'b0;
        // pc_offset_t <= 32'b0;
        // alu_result_t <= 32'b0;
        // rd2_t <= 32'b0;
        // ins_t <= 32'b0;
        // alu_zero_t <= 0;

        // Branch_t <= 0;
        // MemRead_t <= 0;
        // MemWrite_t <= 0;
        // RegWrite_t <= 0;
        // jal_t <= 0;
        // MemtoReg_t <= 2'b00;

        pc_4_o <= 0;
        pc_offset_o <= 0;
        alu_result_o <= 0;
        rd2_o <= 0;
        ins_o <= 0;
        alu_zero_o <= 0;

        Branch_o <= 0;
        MemRead_o <= 0;
        MemWrite_o <= 0;
        RegWrite_o <= 0;
        jal_o <= 0;
        MemtoReg_o <= 0;
    end
    else begin
        // pc_4_t <= pc_4;
        // pc_offset_t <= pc_offset;
        // alu_result_t <= alu_result;
        // rd2_t <= rd2;
        // ins_t <= ins;
        // alu_zero_t <= alu_zero;

        // Branch_t <= Branch;

```

```

        // MemRead_t <= MemRead;
        // MemWrite_t <= MemWrite;
        // RegWrite_t <= RegWrite;
        // jal_t <= jal;
        // MemtoReg_t <= MemtoReg;

        pc_4_o <= pc_4;
        pc_offset_o <= pc_offset;
        alu_result_o <= alu_result;
        rd2_o <= rd2;
        ins_o <= ins;
        alu_zero_o <= alu_zero;

        Branch_o <= Branch;
        MemRead_o <= MemRead;
        MemWrite_o <= MemWrite;
        RegWrite_o <= RegWrite;
        jal_o <= jal;
        MemtoReg_o <= MemtoReg;
    end
end
endmodule

module Forwarding(
    input [31:0] ins_EX,
    input [31:0] ins_MEM,
    input [31:0] ins_WB,
    input RegWrite_MEM, RegWrite_WB,
    output reg [1:0] alu_rs1_mux_signal,
    output reg [1:0] alu_rs2_mux_signal
);

    always@(*) begin
        if(RegWrite_MEM && ins_MEM[11:7]==ins_EX[19:15])
            alu_rs1_mux_signal = 2'b01;
        else if(RegWrite_WB && ins_WB[11:7]==ins_EX[19:15])
            alu_rs1_mux_signal = 2'b10;
        else
            alu_rs1_mux_signal = 2'b00;

        if(RegWrite_MEM && ins_MEM[11:7]==ins_EX[24:20])
            alu_rs2_mux_signal = 2'b01;
        else if(RegWrite_WB && ins_WB[11:7]==ins_EX[24:20])
            alu_rs2_mux_signal = 2'b10;
        else
            alu_rs2_mux_signal = 2'b00;
    end
end

endmodule

module ID_EX(
    input clk,rst,
    input en,
    input [31:0] ins,

```

```

input [31:0] immediate,
input [31:0] pc,
input [31:0] pc_4,
input [31:0] rd1,rd2,
output reg [31:0] ins_o,
output reg [31:0] pc_o,
output reg [31:0] pc_4_o,
output reg [31:0] immediate_o,
output reg [31:0] rd1_o,rd2_o,
input Branch, MemRead, MemWrite, RegWrite, ALUSrc, jal,
input [1:0] ALUop, MemtoReg,
output reg Branch_o, MemRead_o, MemWrite_o, RegWrite_o, ALUSrc_o, jal_o,
output reg [1:0] ALUop_o, MemtoReg_o
);

reg [31:0] ins_t, pc_t, pc_4_t,immediate_t,rd1_t,rd2_t;
reg Branch_t, MemRead_t, MemWrite_t, RegWrite_t, ALUSrc_t, jal_t;
reg [1:0] ALUop_t, MemtoReg_t;

always@(posedge clk or posedge rst) begin
    if(rst || en) begin
        // ins_t <= 32'b0;
        // pc_t <= 32'b0;
        // pc_4_t <= 32'b0;
        // immediate_t <= 32'b0;
        // rd1_t <= 32'b0;
        // rd2_t <= 32'b0;
        // Branch_t <= 0;
        // MemRead_t <= 0;
        // MemWrite_t <= 0;
        // RegWrite_t <= 0;
        // ALUSrc_t <= 0;
        // jal_t <= 0;
        // ALUop_t <= 2'b00;
        // MemtoReg_t <= 2'b00;

        ins_o <= 0;
        pc_o <= 0;
        pc_4_o <= 0;
        immediate_o <= 0;
        rd1_o <= 0;
        rd2_o <= 0;
        Branch_o <= 0;
        MemRead_o <= 0;
        MemWrite_o <= 0;
        RegWrite_o <= 0;
        ALUSrc_o <= 0;
        jal_o <= 0;
        ALUop_o <= 0;
        MemtoReg_o <= 0;
    end
    else begin
        // ins_t <= ins;
        // pc_t <= pc;

```

```

        // pc_4_t <= pc_4;
        // immediate_t <= immediate;
        // rd1_t <= rd1;
        // rd2_t <= rd2;
        // Branch_t <= Branch;
        // MemRead_t <= MemRead;
        // MemWrite_t <= MemWrite;
        // RegWrite_t <= RegWrite;
        // ALUsrc_t <= ALUsrc;
        // jal_t <= jal;
        // ALUop_t <= ALUop;
        // MemtoReg_t <= MemtoReg;

        ins_o <= ins;
        pc_o <= pc;
        pc_4_o <= pc_4;
        immediate_o <= immediate;
        rd1_o <= rd1;
        rd2_o <= rd2;
        Branch_o <= Branch;
        MemRead_o <= MemRead;
        MemWrite_o <= MemWrite;
        RegWrite_o <= RegWrite;
        ALUsrc_o <= ALUsrc;
        jal_o <= jal;
        ALUop_o <= ALUop;
        MemtoReg_o <= MemtoReg;
    end
end
endmodule

module IF_ID(
    input clk,rst,
    input [31:0] ins,
    input [31:0] pc,
    input [31:0] pc_4,
    input en,
    input jump,
    output reg [31:0] ins_o,
    output reg [31:0] pc_o,
    output reg [31:0] pc_4_o
);

    reg [31:0] ins_t, pc_t, pc_4_t;

    always@(posedge clk or posedge rst) begin
        if(rst || jump) begin
            // ins_t <= 32'b0;
            // pc_t <= 32'b0;
            // pc_4_t <= 32'b0;

            ins_o <= 0;
            pc_o <= 0;
            pc_4_o <= 0;
        end
    end
end

```



```

        end
        else if (en) begin
            // ins_t <= ins;
            // pc_t <= pc;
            // pc_4_t <= pc_4;

            ins_o <= ins;
            pc_o <= pc;
            pc_4_o <= pc_4;
        end
    end
endmodule

module Immgen(
    input [31:0] instruction,
    output reg [31:0] immediate
);
    always @(*) begin
        if(instruction[6:0]==7'b0010011)    //addi
            immediate = {{20{instruction[31]}},instruction[31:20]};
        else if(instruction[6:0]==7'b0000011)    //lw
            immediate = {{20{instruction[31]}},instruction[31:20]};
        else if(instruction[6:0]==7'b0100011)    //sw
            immediate =
{{20{instruction[31]}},instruction[31:25],instruction[11:7]};
        else if(instruction[6:0]==7'b1100011)    //beq,blt
            immediate =
{{20{instruction[31]}},instruction[31],instruction[7],instruction[30:25],instructi
on[11:8]};
        else if(instruction[6:0]==7'b1101111)    //jal
            immediate =
{{12{instruction[31]}},instruction[31],instruction[19:12],instruction[20],instruct
ion[30:21]};
        else if(instruction[6:0]==7'b1100111)    //jalr
            immediate = {{20{instruction[31]}},instruction[31:20]};
        else if(instruction[6:0]==7'b0010111)    //auipc
            immediate = {instruction[31:12],12'b0};
        else
            immediate = instruction;
    end
endmodule

module MEM_WB(
    input clk,rst,
    input [31:0] alu_result,
    input [31:0] ins,
    input [31:0] MemReadData,
    input [31:0] pc_4,
    output reg [31:0] alu_result_o,
    output reg [31:0] ins_o,
    output reg [31:0] MemReadData_o,
    output reg [31:0] pc_4_o,

    input RegWrite,

```

```

    input [1:0] MemtoReg,
    output reg RegWrite_o,
    output reg [1:0] MemtoReg_o
);

reg [31:0] alu_result_t, ins_t, MemReadData_t, pc_4_t;

reg RegWrite_t;
reg [1:0] MemtoReg_t;

always@(posedge clk or posedge rst) begin
    if(rst) begin
        // alu_result_t <= 32'b0;
        // ins_t <= 32'b0;
        // MemReadData_t <= 32'b0;
        // pc_4_t <= 32'b0;

        // RegWrite_t <= 0;
        // MemtoReg_t <= 2'b00;

        alu_result_o <= 0;
        ins_o <= 0;
        MemReadData_o <= 0;
        pc_4_o <= 0;
        RegWrite_o <= 0;
        MemtoReg_o <= 0;
    end
    else begin
        // alu_result_t <= alu_result;
        // ins_t <= ins;
        // MemReadData_t <= MemReadData;
        // pc_4_t <= pc_4;
        // RegWrite_t <= RegWrite;
        // MemtoReg_t <= MemtoReg;

        alu_result_o <= alu_result;
        ins_o <= ins;
        MemReadData_o <= MemReadData;
        pc_4_o <= pc_4;
        RegWrite_o <= RegWrite;
        MemtoReg_o <= MemtoReg;
    end
end

endmodule

module mux2to1 (
    input [31:0] a, b,
    input sel,
    output reg [31:0] out
);
always@(*) begin
    case(sel)
        1'b0: out = a;

```

```

        1'b1: out = b;
    endcase
end
endmodule

module mux3to1(
    input [31:0] a, b, c,
    input [1:0] sel,
    output reg [31:0] out
);
    always@(*) begin
        case(sel)
            2'b00: out = a;
            2'b01: out = b;
            2'b10: out = c;
            default: out = a;
        endcase
    end
endmodule

module pc(
    input [31:0] in,
    input rst,
    input clk,
    input en,
    output reg [31:0] out
);
    always @(posedge clk or posedge rst) begin
        if (rst)
            out <= 32'h3000;
        else if (en)
            out <= in;
        end
    end
endmodule

module register(
    input clk,
    input rst,
    input w_en,
    input [4: 0] addr1,
    input [4: 0] addr2,
    input [4: 0] addr3,
    input [31: 0] w_data3,
    output wire [31:0] rd_data1,
    output wire [31:0] rd_data2,
    input [31:0] debug_addr,
    output wire [31:0] debug_data
);
    reg [31: 0] RegFile[0:31];
    integer i;
    assign rd_data1 = (addr1 == 5'b0) ? 32'b0 : RegFile[addr1];
    assign rd_data2 = (addr2 == 5'b0) ? 32'b0 : RegFile[addr2];
    assign debug_data = (debug_addr == 5'b0) ? 32'b0 : RegFile[debug_addr];

```

```

always@(negedge clk or posedge rst) begin
    if (rst) begin
        for (i = 0; i < 32; i = i + 1)
            RegFile[i][31:0] <= 32'b0;
        end
    else if (w_en == 1'b1 && addr3 != 5'b0) begin
        RegFile[addr3] <= w_data3;
    end
end

endmodule

module shiftleft(
    input [31:0] in,
    output reg [31:0] out
);
    always@(*)
        out = in << 1;
endmodule

module stall(
    input MemRead_EX, Branch_ID, RegWrite_EX, RegWrite_MEM, RegWrite_WB,
    input [31:0] ins_EX,
    input [31:0] ins_ID,
    input [31:0] ins_MEM,
    input [31:0] ins_WB,
    output reg pc_write, IF_ID_write, control_mux, jump
);
    always@(*) begin
        if(MemRead_EX &&
(ins_EX[11:7]==ins_ID[19:15]||ins_EX[11:7]==ins_ID[24:20])) begin
            pc_write = 0;
            IF_ID_write = 0;
            control_mux = 1;
            jump = 0;
        end
        else if(Branch_ID && RegWrite_EX &&
(ins_EX[11:7]==ins_ID[19:15]||ins_EX[11:7]==ins_ID[24:20])) begin
            pc_write = 0;
            IF_ID_write = 0;
            control_mux = 1;
            jump = 0;
        end
        else if(Branch_ID && RegWrite_MEM &&
(ins_MEM[11:7]==ins_ID[19:15]||ins_MEM[11:7]==ins_ID[24:20])) begin
            pc_write = 0;
            IF_ID_write = 0;
            control_mux = 1;
            jump = 0;
        end
        // else if(Branch_ID && RegWrite_WB &&
(ins_WB[11:7]==ins_ID[19:15]||ins_WB[11:7]==ins_ID[24:20])) begin
            // pc_write = 0;
            // IF_ID_write = 0;

```

```
//      control_mux = 1;
//      jump = 0;
// end
else if(Branch_ID) begin
    pc_write = 1;
    IF_ID_write = 1;
    control_mux = 0;
    jump = 1;
end
else begin
    pc_write = 1;
    IF_ID_write = 1;
    control_mux = 0;
    jump = 0;
end
end
endmodule
```