2.1

(1)
$$A \oplus 0 = A$$

А	$A\oplus 0$
0	0
1	1

(4) $A \oplus A' = 1$

А	$A \oplus A'$
0	1
1	1

$$(7)A \oplus B' = (A \oplus B)' = A \oplus B \oplus 1$$

Α	В	$A \oplus B'$	$(A \oplus B)'$	$A\oplus B\oplus 1$
0	0	1	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	1	1

2.3

$$Y_1 = \overline{ABC} + \overline{AB}C + A\overline{B}C + A\overline{B}C + ABC$$

$$Y_2 = \overline{ABC}D + \overline{AB}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}CD + A\overline{B}CD + AB\overline{C}D + ABC\overline{D}$$

2.5

(1)

А	В	С	D	Y_1
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(2)

Α	В	С	D	Y_2
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

2.7

(a)

$$Y_1 = \overline{\overline{A + B}C} \oplus \overline{\overline{C}D}$$

(b)

$$Y_2 = \overline{\overline{A}\overline{B}}E + \overline{\overline{B}CD}E$$

2.8

С	В	А	Υ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$Y = AB\overline{C} + A\overline{B}C + \overline{A}BC$$

2.10

(1)
$$Y = \sum m(1,3,5,7)$$

(4)
$$Y = \sum m(3,6,7,11,12,13,14,15)$$

(6)
$$Y = \sum m(1, 2, 4, 5, 6, 7, 8, 9, 10, 11, 13, 14)$$

2.11

(2)
$$Y=\prod m(0,2,6)$$

(5)
$$Y = \prod m(0, 3, 5)$$

2.12

(3)
$$AB' + AC + BC = AB' + ABC + AB'C + BC = AB' + BC$$

$$(6)ABD + AB'CD' + AC'DE + A = A$$

2.13

(2)
$$Y = AB'C + A' + B + C' = \sum m(0, 1, 2, 3, 4, 5, 6, 7) = 1$$

$$Y = BC' + ABC'E + B'(A'D' + AD)' + B(AD' + A'D) = BC' + B'(A \odot D)' + B(A \oplus D) = BC'$$